



CE232 DIGITAL SYSTEM

# Topic 10. Simplification of Sequential Circuit

---

Prepared by Nabila Husna Shabrina

Contact : [nabila.husna@umn.ac.id](mailto:nabila.husna@umn.ac.id)

# Subtopic

---

**10.2 Moore and  
Mealy State  
Diagram**

---

**10.2 State  
Diagram  
Simplification**





“

# 10.1 Moore and Mealy State Diagram

# 10.1 Moore and Mealy State Diagram

---


There are two models developed to representing sequential circuit

- Moore circuit/ Moore state machine : the output is the function of present state
- Mealy circuit/Mealy state machine : the output is the function of present state as well as input

→ The difference Is only in the way the output is generated


# 10.1 Moore and Mealy State Diagram

## Moore vs Mealy

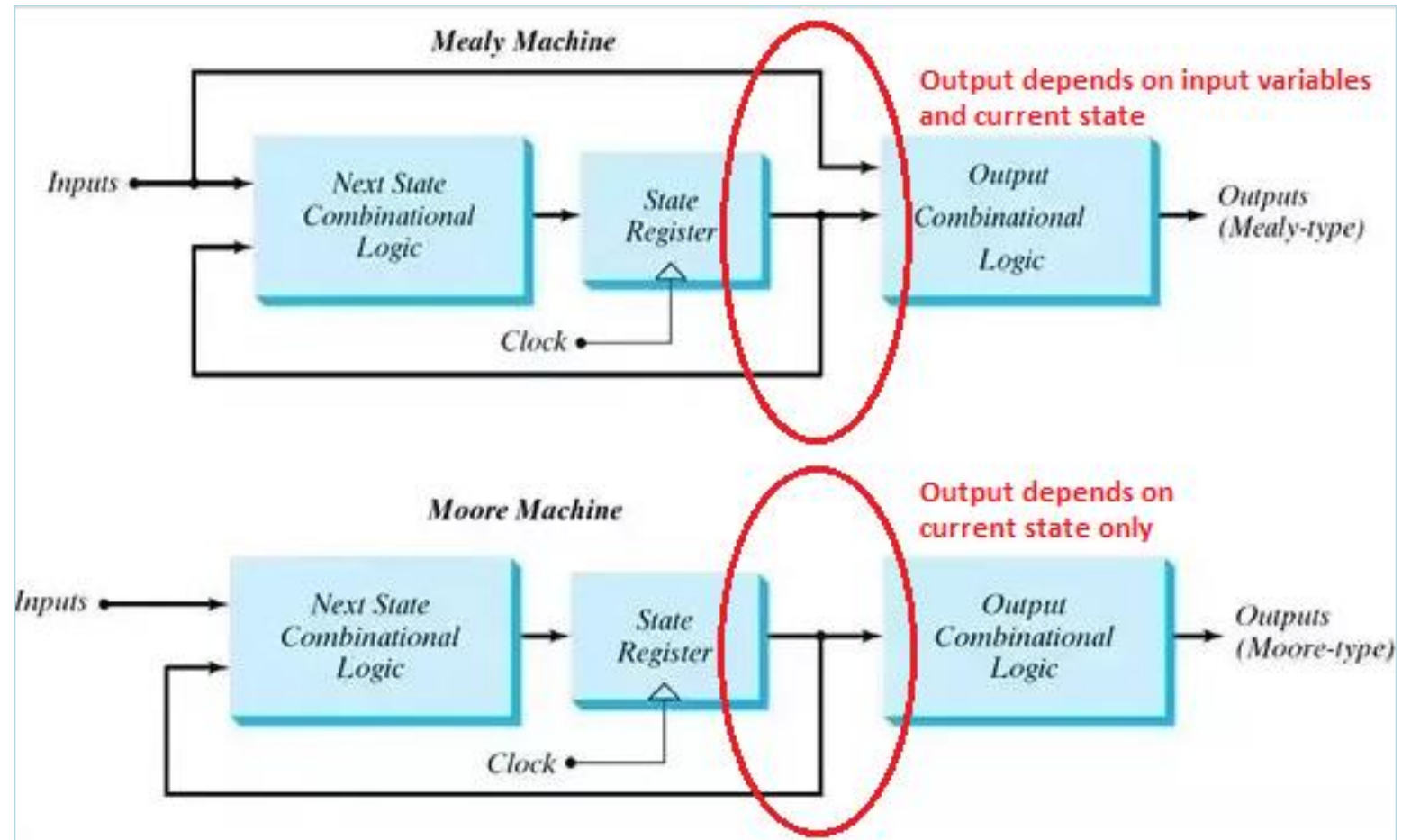

# 10.1 Moore and Mealy State Diagram

Example of Moore circuit

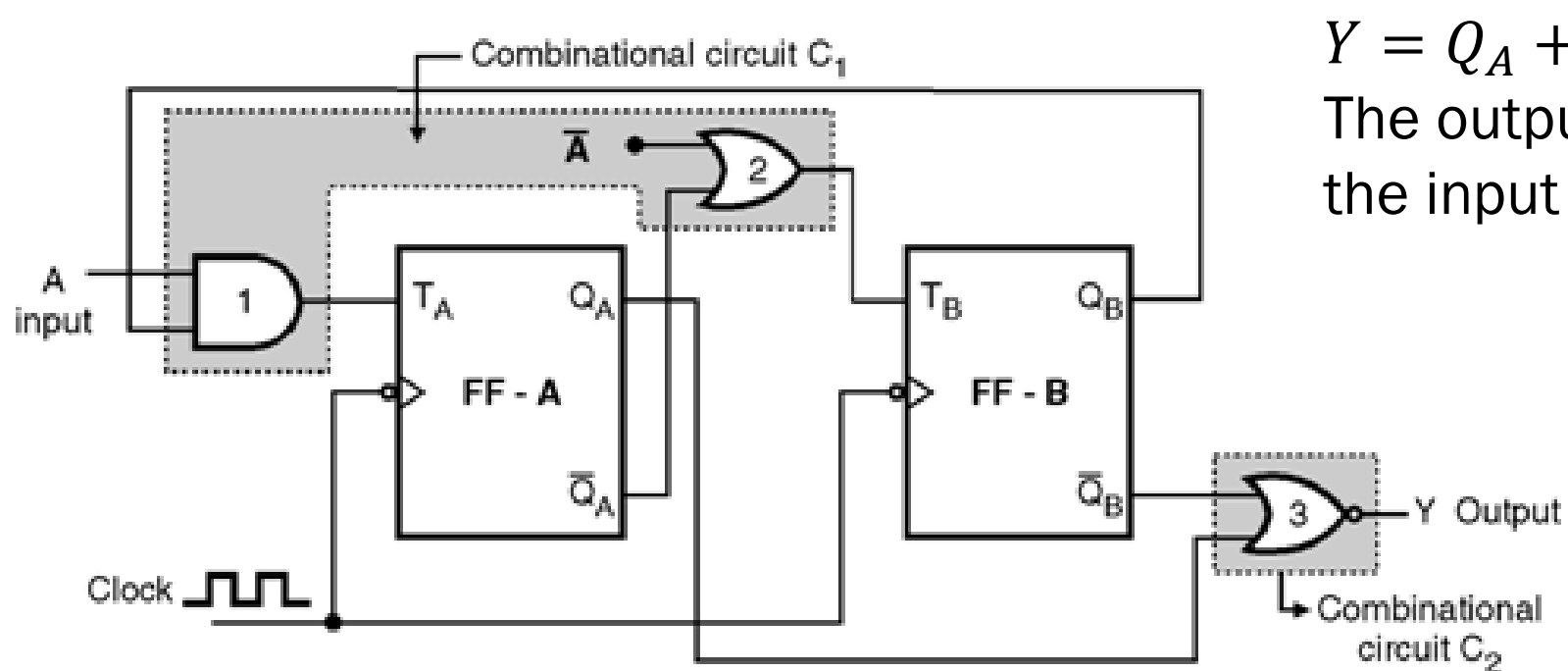


$$Y = Q_A + \overline{Q_B}$$

The output independent of the input A

# 10.1 Moore and Mealy State Diagram


Example of Moore state diagram

Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

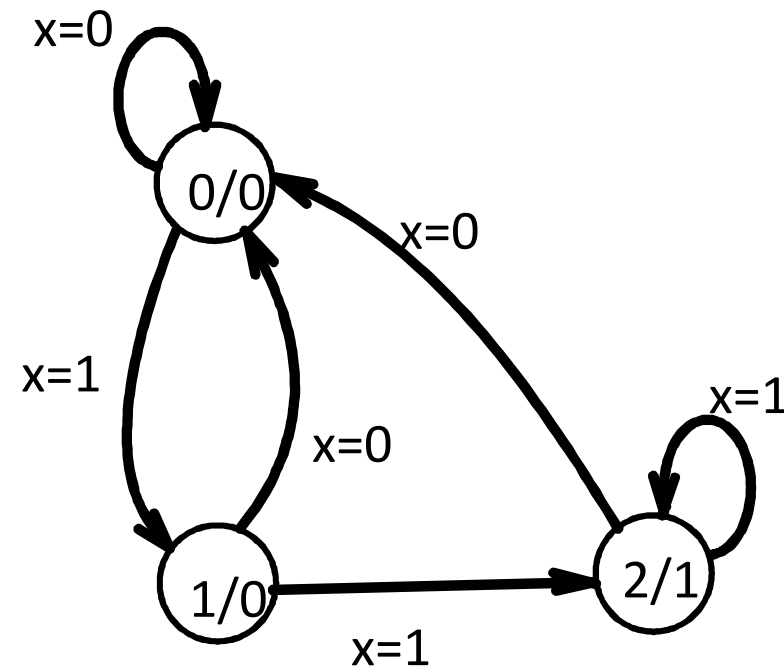

# 10.1 Moore and Mealy State Diagram

Example of Moore state diagram

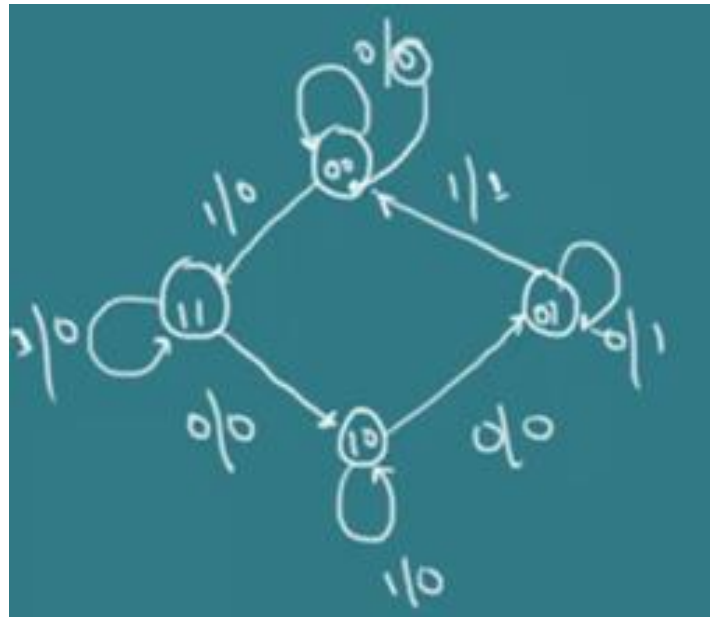


PS	NS		OUTPUT	
	X=0	X=1	X=0	X=1
00	00	11	0	0
01	01	00	1	1
10	01	10	0	0
11	10	11	0	0




# 10.1 Moore and Mealy State Diagram

Example of Moore state diagram

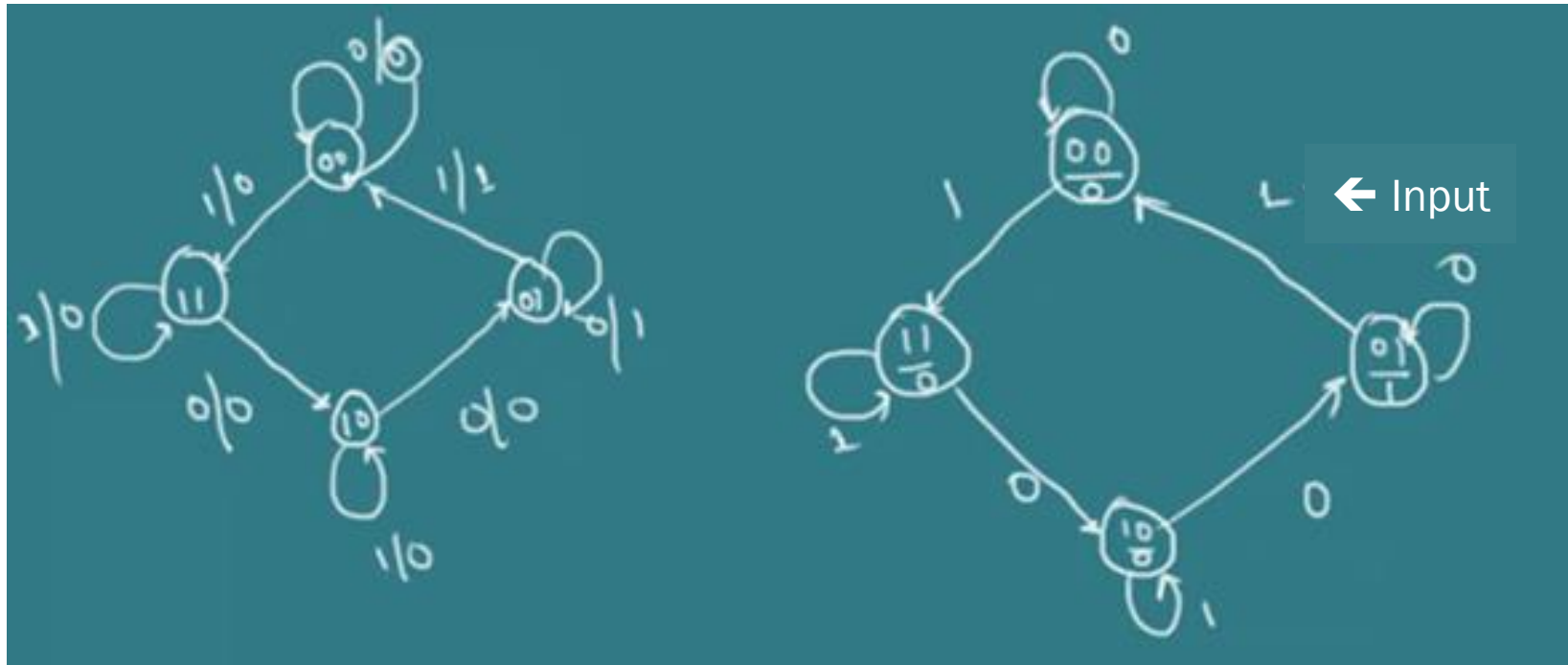


## Example of Mealy circuit

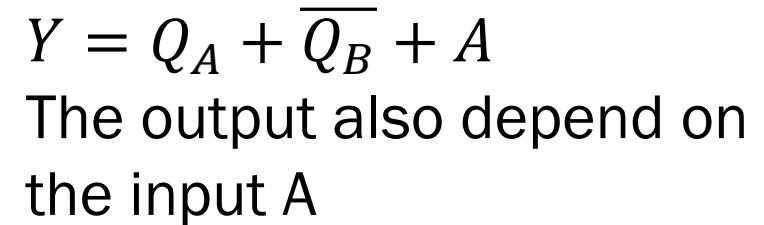

# 10.1 Moore and Mealy State Diagram

Example of Mealy state diagram

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

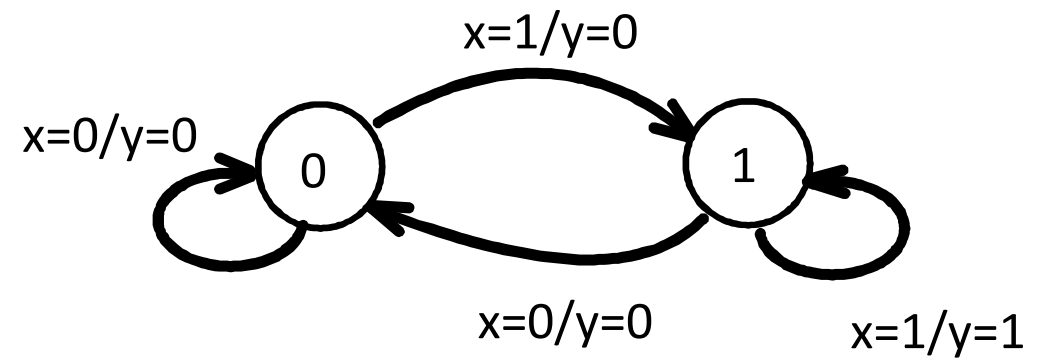

The slide features several large, overlapping geometric shapes in teal, yellow, and green, primarily located in the top right and bottom left corners. A large black quotation mark is positioned to the left of the title.

“

## 10.2 State Diagram Simplification

## 10.2 State Diagram Simplification



---

### Equivalent state

- Two states are equivalent if their **response** for each possible input sequence is an **identical output** sequence.
- Alternatively, two states are equivalent if **their outputs** produced for each input symbol is **identical** and **their next states** for each input symbol are the **same or equivalent**.

## 10.2 State Diagram Simplification



---


### Step

1. Make state diagram
2. Find the equivalent states, remove the redundant state
3. Make a reduce state table
4. Construct the simplified state diagram

## 10.2 State Diagram Simplification


Example.

Simplified the given state diagram

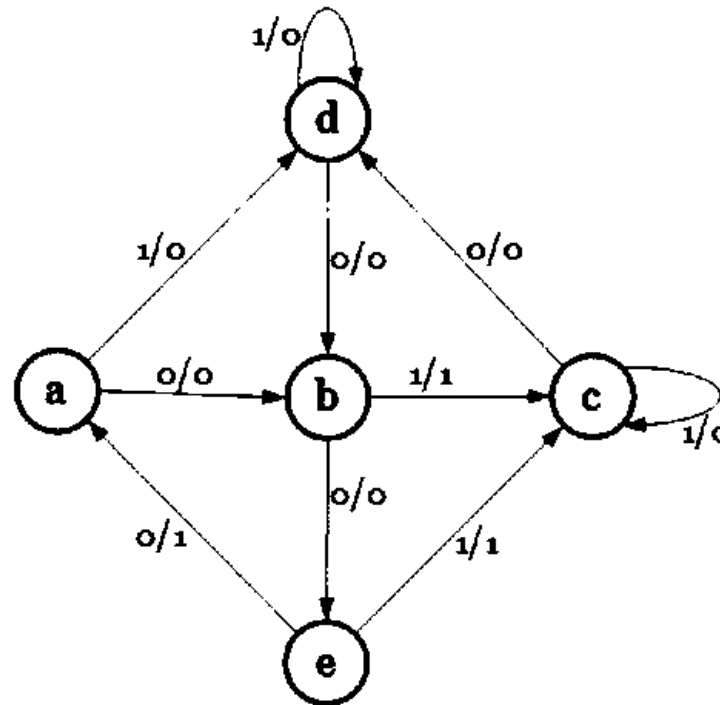

# 10.2 State Diagram Simplification

Step 1. Make state diagram

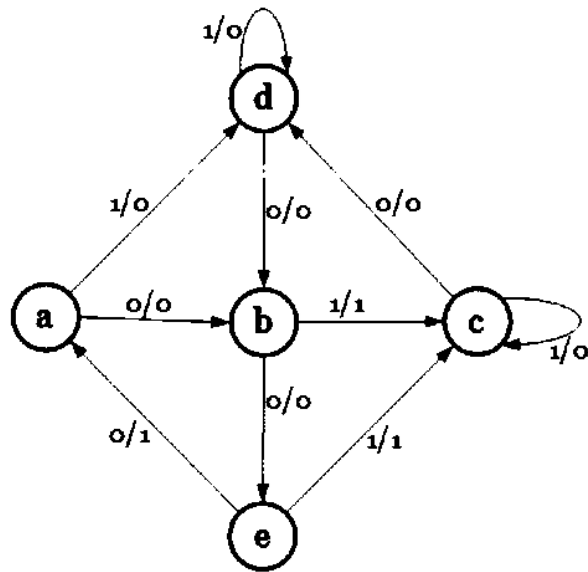

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	b	d	0	0
b	e	c	0	1
c	d	c	0	0
d	b	d	0	0
e	a	c	1	1



## 10.2 State Diagram Simplification

Step 2. Find the equivalent states, remove the redundant state

Equivalent states

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	b	d	0	0
b	e	c	0	1
c	d	c	0	0
d	b	d	0	0
e	a	c	1	1

A and D are found as equivalent states. So, **replace D by A and remove D**


## 10.2 State Diagram Simplification

Step 3. Make a reduce state table

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	b	a	0	0
b	e	c	0	1
c	a	c	0	0
e	a	c	1	1
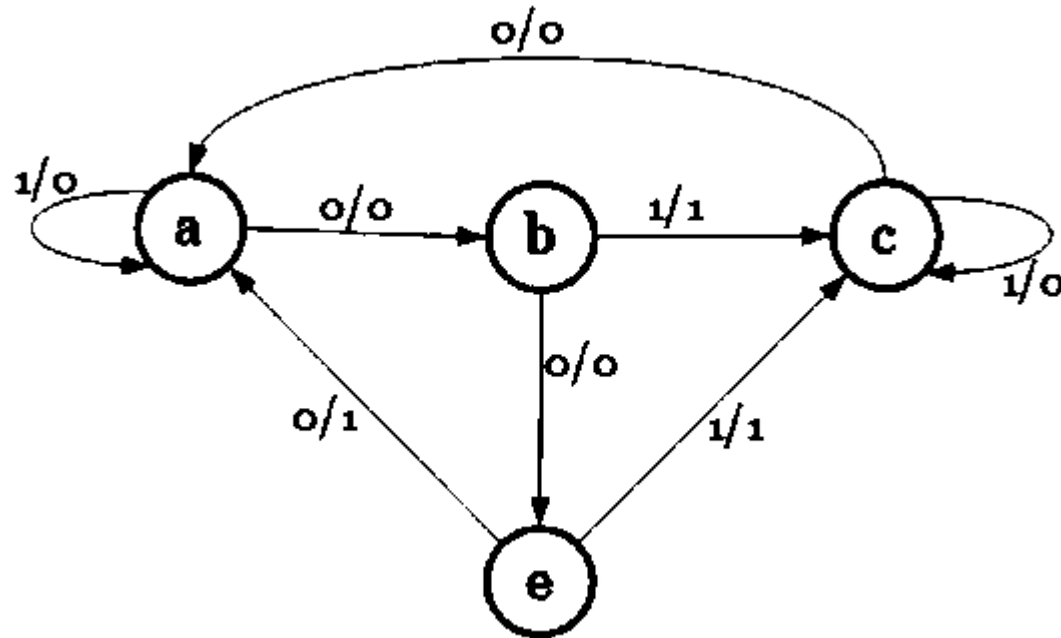
## 10.2 State Diagram Simplification

Step 4. Construct the simplified state diagram



## 10.2 State Diagram Simplification

Example.

Construct a simplified state diagram from the following state table.

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	b	c	0	0
b	b	d	0	0
c	b	a	0	0
d	e	c	1	0
e	b	d	0	0

## 10.2 State Diagram Simplification

Answer :

Find the equivalent states, remove the redundant state

Equivalent states


Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	b	c	0	0
b	b	d	0	0
c	b	a	0	0
d	e	c	1	0
e	b	d	0	0

D and E are found as equivalent states. So, replace E by B and remove E

## 10.2 State Diagram Simplification

Make the simplified state table and state diagram


Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	b	c	0	0
b	b	d	0	0
c	b	a	0	0
d	b	c	1	0

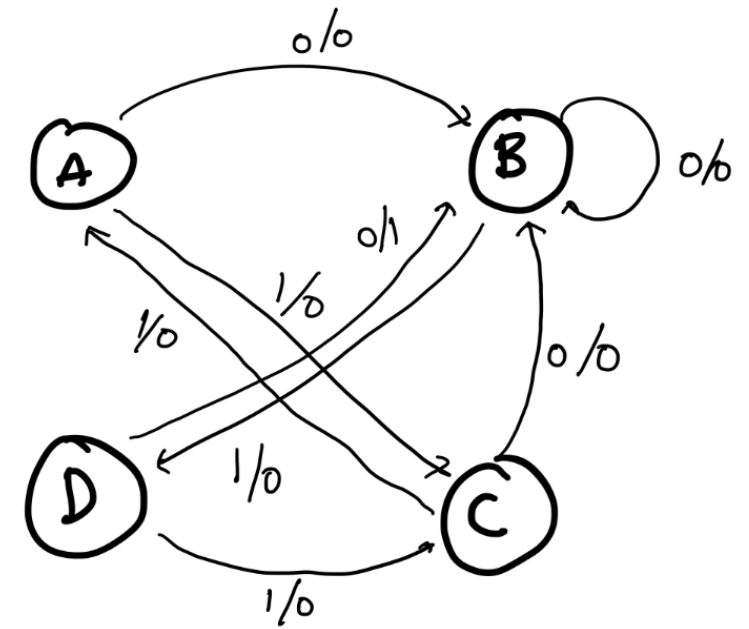

## 10.2 State Diagram Simplification

Assignment.

Simplified the given  
state diagram

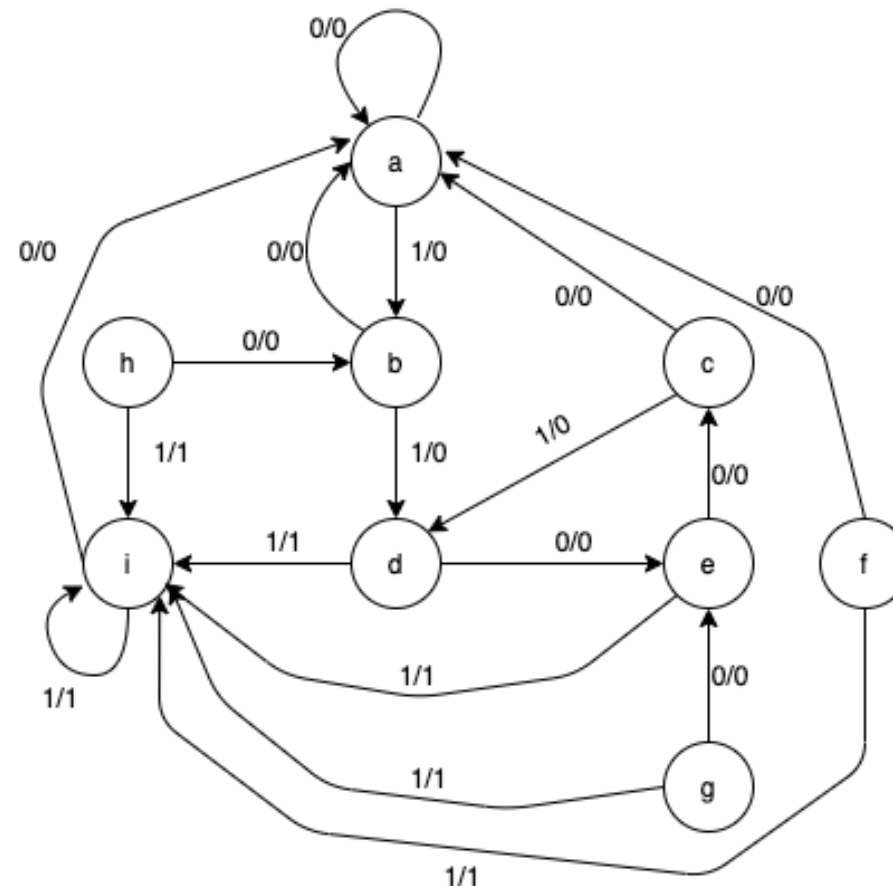



# References

---

M. Morris Mano, Digital Design, 5<sup>th</sup> ed, Prentice Hall, 2012, Chapter 5



The slide features several large, overlapping geometric shapes in teal, yellow, and green, primarily located in the top right and bottom left corners. The main text is centered in a bold, black, sans-serif font.

# **Next Topic : Design of Sequential Circuit**